

## Tutorial 3, Sep 27, 2023

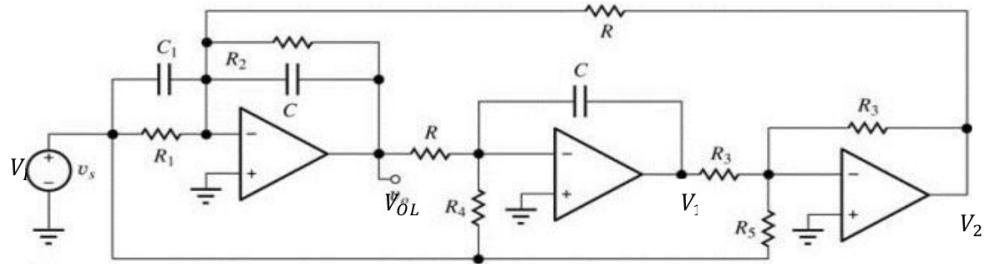


Figure 1: Example problem: two integrator biquad.

- Example: find the transfer function of the above
  - Replace  $C_1, R_1$  by impedance  $Z_a = \frac{R}{sR_1C_1 + 1}$
  - Replace  $C, R_2$  by impedance  $Z_2 = \frac{R_2}{sR_2C + 1}$
  - Replace  $R$  by impedance  $Z_b$
  - At the first op-amp we have an inverting summing amplifier
    - \* We don't need to worry about  $R_4$  and  $R_5$  since they just contribute to  $V_I$
    - \*  $V_{OL} = -\frac{Z_2}{Z_a}V_I - \frac{Z_2}{Z_b}V_2 = -\frac{R_2(sR_2C_1 + 1)}{(sR_2C + 1)R_1}V_I - \frac{R_2}{(sR_2C + 1)R}V_2$
  - $V_2 = -\frac{R_3}{R_5}V_I$ 
    - \* Sub in  $V_2$  to get  $V_{OL}$  in terms of  $V_I$  and  $V_I$
  - $V_1 = -\frac{\frac{1}{sC}}{R}V_{OL} - \frac{\frac{1}{sC}}{R_4}V_I$
  - ... a bunch of nasty algebra later

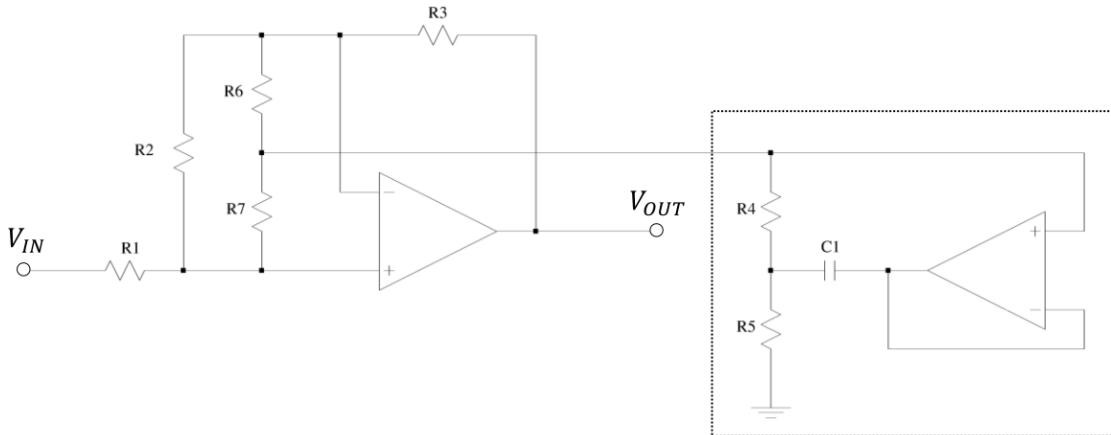


Figure 2: Example problem.

- Example: find the transfer function of the circuit above
  - We will model the sub-circuit in the box as an equivalent impedance connected to ground
  - First find  $Z_{eq}$ 
    - \* Assume a voltage of  $V_{in}$  at the top node
    - \* Since this is an ideal op-amp, the inverting input and output are also at  $V_{in}$  and no current flows into the noninverting input
    - \* Node equation at  $A$ , the node between the resistors:  $\frac{V_A - V_{in}}{R_4} + \frac{V_A}{R_5} + \frac{V_A - V_{in}}{\frac{1}{sC_1}}$

- \*  $V_A \left( \frac{R_5 + R_4 + sR_4R_5C_1}{R_5R_4} \right) = V_{in} \left( \frac{1 + sR_4C_1}{R_4} \right)$
- \*  $\frac{V_A}{V_{in}} = \frac{R_5 + sR_4C_1R_5}{R_5 + R_4 + sR_4R_5C_1}$
- \* If we have an input current  $I_{in}$ , then  $I_{in} = \frac{V_{in} - V_A}{R_4}$  which we can substitute  $V_A$
- \*  $Z_{eq} = \frac{V_{in}}{I_{in}} = \frac{1}{R_5 + R_4 + sR_4R_5C_1}$